Name:Tafadzwa Chiripanyanga

Date:3/19/2023

Question 1

a)

A	В	F
0	0	0
0	1	1
1	0	1
1	1	0

B)

Χ	0	F
1	0	1
0	0	0

b)


Х	X'	(x')'
0	1	0
1	0	1

c)


Х	у	Z	(x+y)+z	x+(y+z)
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	1
1	0	0	1	1
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

A)

Question 2

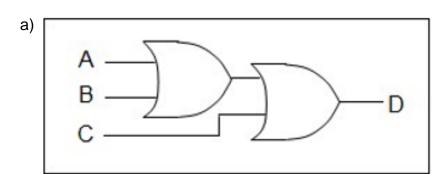


D=[(A+B)+C]

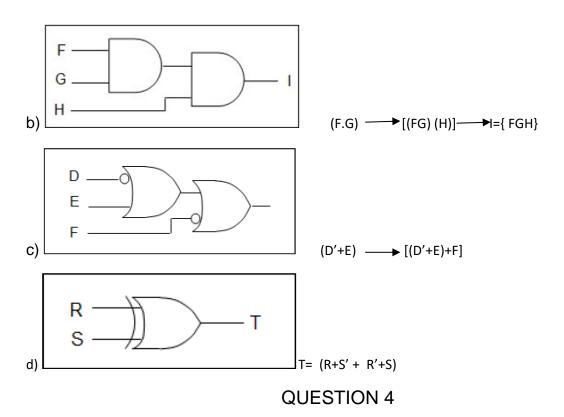

- a) Overflow is when the number of bits (or data) exceeds the storage capacity of a computer's memory .
- b) An overflow is handled through taking it (digit)and adding it back to the right most digit (for example if the digit is one , you take it from the front and add it to the last digit (rightmost digit) of your bits)


C)


a) 62+47 =131

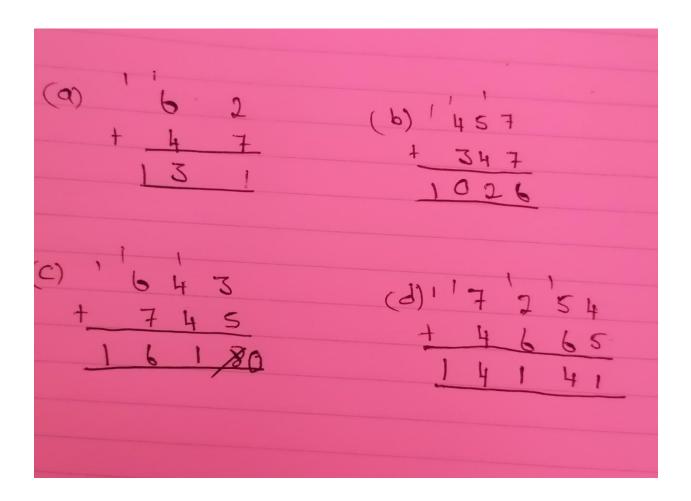


- b)457+347=1026
- c)643+745=16180
- d) 7254+4665=141441

Question 5

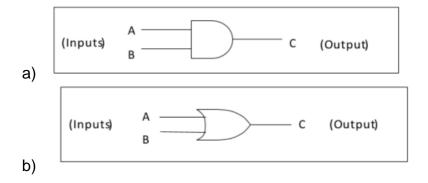

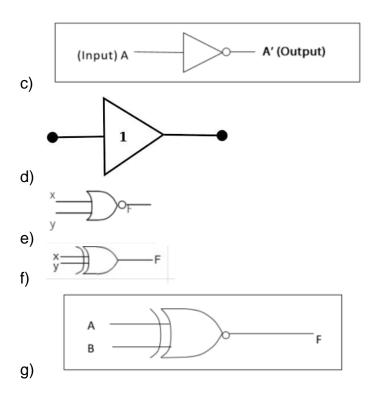

Question6

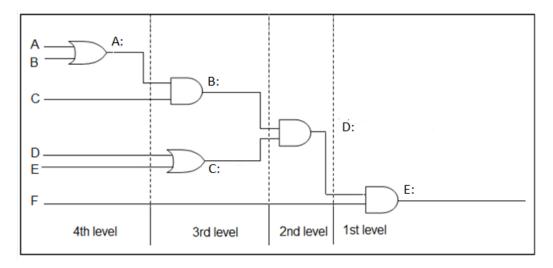

A:(A+B)

B:(C) (A+B)

```
C:(D+E)
D:(C)(A+B)(D+E)
E:(C)(A+B)(D+E)(F)
                                    Question 7
a) F = (ab)(cd')(a')
     =(a a') (b c) (d')
    =0
b) F = xzy + xzy' + x'z
     =x (zy+zy') +x'z
     =x(z(y+y')+x'z
     =x(z(1))+x'z
     =xz+x'z
     =Z(X+X')
     =Z
c) F = ab'c + ac'(b + a') + a'b'c
   =ab'c +ac'b +ac'a' + a'b'c
   =ab'c +c'(ab+aa')+a'b'c
   =ab'c +c'ab +a'b'c
   =c(ab'+a'b')+c'ab
   =c(b'(a+a'))+c'ab
   =cb'+c'ab
d) F = xwy' + z'yxw + wxyz + yx'zw
   =w(xy'+z'yx+xyz+yx'z)
   =w(x(y'+z'y+yz)+yx'z)
```

=w(x(y')(y(z'+z))+yx'z)


a) F = ABC + AB'C + AB'C'

Α	В	С	B'	C'	ABC	AB'C	AB'C'	F
0	0	0	1	1	0	0	0	0
0	0	1	1	0	0	0	0	0
0	1	0	0	1	0	0	0	0
0	1	1	0	0	0	0	0	0
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0
1	1	1	0	0	1	0	0	0

ABC+AB'C+AB'C'

$$=A(BC+B'C+B'C')$$

$$=A(BC+B'(C+C'))$$

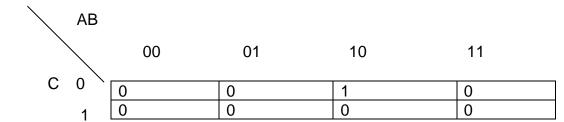

b) F = A'B'C + A'BC + ABC' + ABC

Α	В	С	A'	B'	C'	A'B'C	A'BC	ABC'	ABC	F
0	0	0	1	1	1	0	0	0	0	0
0	0	1	1	1	0	1	0	0	0	1
0	1	0	1	0	1	0	0	0	0	0
0	1	1	1	0	0	0	1	0	0	1
1	0	0	0	1	1	0	0	0	0	0
1	0	1	0	1	0	0	0	0	0	0
1	1	0	0	0	1	0	0	1	0	1
1	1	1	0	0	0	0	0	0	1	1

C		00	01	10	11
C	U	0	0	0	1
	1	1	1	0	1

F = A'B'C + A'BC + ABC' + ABC

=C(A'B'+A'B+AB)+ABC'

=C(A'(B'+B)+AB)+ABC'

=C(A'+AB)+ABC

=CA'+CAB+ABC'


=CA'+AB(C+C')

=CA'+AB

QUESTION9

LAD\ OPTI	ONS	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16
C1	Red dress	Υ	Υ	Υ	Υ	Υ	Υ	Υ	Υ	N	Ν	N	N	N	N	N	Ν
C2	A cap	Υ	Υ	Υ	Υ	N	N	N	N	Υ	Υ	Υ	Υ	N	N	N	N
C3	A shirt	Υ	Υ	N	N	Υ	Υ	N	N	Υ	Υ	N	N	Υ	Υ	N	N
C4	Mini skirt	Υ	Ν	Υ	N	Υ	N	Υ	N	Υ	Ν	Υ	N	Υ	N	Υ	N
A1	Shirt	Χ				Χ				Χ				Χ			
A2	mini skirt	Χ				Χ				Χ				Χ			
А3	Pair of shoes				Χ		Χ	Χ	Χ		Χ	Χ	Χ	Χ	Χ	Χ	Χ
A4	Two pairs of shoes	Х	Х	X		X				X							

Question 10

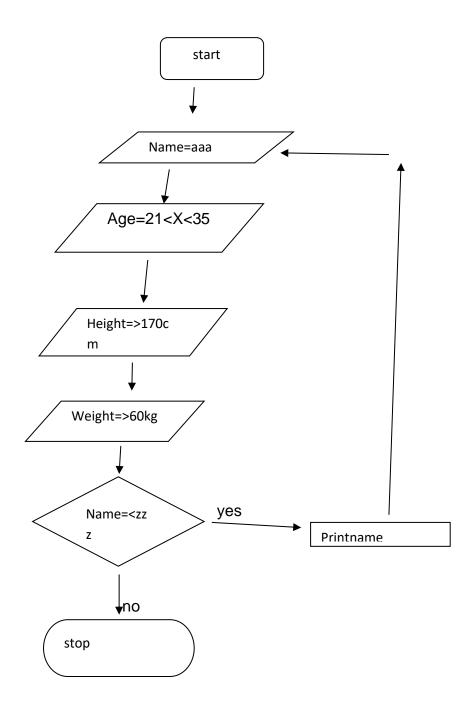

REFRENCING

https://youtu.be/RO5alU6PpSU

https://youtu.be/JQBRzsPhw2w















Boolean Algebra 2 – Boolean Algebra 1 – 5 Truth Table to Simplifying Complex EThe Laws of Boolean /Boolean Expression.m Example 1.mp4

4 Karnaugh Maps -

3 Karnaugh Maps -Introduction.mp4



Boolean Expression Represented as a Trul



PRFU_Programming Fundamentals-Process